

EXHIBIT B

[FCC Ref. 2.1033(b)(4)]

"Description of Circuit Functions"

2-6920M Circuit Description :

The following circuit description for THOMSON model 2-6920M is base on the circuit diagram and block diagram of 2-6920M.

2-6920M Handset :

1. Receiving Path

The receiving path is established by below sections.

③ Low Noise Amplifier (LNA)

FM signal filtering by the duplexer, and input to tuning amplifier Q555. Then filtering once more by band pass filter DF502, and input to 2nd tuning amplifier Q512 before output to mixer.

③ Mixer

Mixer is included Q520, and local oscillator Q506 & 504, which is controlled by the PLL U501. The IF (10.7MHz) is filtering by a ceramic filter CF501, the filtered IF will input to IF amplifier.

③ IF amplifier

IF amplifier is built with Q515 & Q8. Amplified IF is filtering again by a ceramic filter CF1, the filtered IF will input to FM demodulator.

③ FM demodulator and expandor

The IF is demodulate by quadrate coil T1, then the recovered audio is input to the expandor for de-emphasis, before output to the handset speaker through audio amplifier.

2. Transmitting Path

The transmitting path is established by below sections.

③ Mic amplifier and compressor

Audio pick up by handset microphone is amplified by internal mic amplifier of U1, then input to compressor for pre-emphasis, before input to the modulator (Tx VCO).

③ Modulator and Tx VCO

The transmit VCO is constructed by Q509 & Q503, which is controlled by PLL of U501. Both audio and data signal input to the transmit VCO will cause a frequency modulation progress.

③ RF power amplifier

FM signal is amplified by Q510 and fit to the antenna through duplexer.

2-6920M Base Unit :

1. Receiving Path

The receiving path is established by below sections.

③ Low Noise Amplifier (LNA)

FM signal filtering by the duplexer, and input to tuning amplifier Q555. Then filtering once more by band pass filter DF502, and input to 2nd tuning amplifier Q512 before output to mixer.

③ Mixer

Mixer is included Q520, and local oscillator Q506 & 504, which is controlled by the PLL U501. The IF (10.7MHz) is filtering by a ceramic filter CF501, the filtered IF will input to IF amplifier.

③ IF amplifier

IF amplifier is built with Q515 & Q8. Amplified IF is filtering again by a ceramic filter CF1, the filtered IF will input to FM demodulator.

③ FM demodulator and expandor

The IF is demodulate by quadrate coil T1, then the recovered audio is input to the expandor for de-emphasis, before output to the handset speaker through audio amplifier.

2. Transmitting Path

The transmitting path is established by below sections.

③ Mic amplifier and compressor

Audio input from line interface is amplified by internal mic amplifier of U1, then input to compressor for pre-emphasis, before input to the modulator (Tx VCO).

③ Modulator and Tx VCO

The transmit VCO is constructed by Q509 & Q503, which is controlled by PLL of U501. Both audio and data signal input to the transmit VCO will cause a frequency modulation progress.

③ RF power amplifier

FM signal is amplified by Q510 and fit to the antenna though duplexer.

3. Telephone line interface

The telephone line interface circuit is established by below sections.

③ Audio power amplifier

Q2 & Q5 are built as a push-pull power amplifier, according to high current output requirement for line interface.

③ Line relay & isolation transformer

T4 is the line isolation transformer, both audio input and output is though this transformer. RL1 is the reed relay for line seize, which is controlled Q3.

③ Ring detect circuit

IC2 is used as a differential amplifier for pick up the ring signal, which is input though two 20M ohm resistor (R44 and R45) as an isolation from the line.

2-6920M digital security coding system :

The handset and base unit of 2-6920M will exchange a random generated 16 bits digital security code, when every time the handset put on the charging cradle of base unit. This is to FCC Part 15.214(d) requirement.